

EES Klausurrechnen

1.) a) $U_V = 3,7 \text{ V} \cdot 3 = 11,1 \text{ V}$

$> 5 \text{ V}$

$U_{\text{bat}} = f(\text{SOC})$

$\neq \text{const.}$



b) $2C \hat{=} 6 \text{ A}, T_{\text{lade}} = 30 \text{ min}$


c) $U_{\text{bat max}} = 3,4 \text{ V}$

$U_{\text{bat min}} = 3,3 \text{ V}$

$U_A = D U_E$

$D_{\text{min}} = \frac{5}{9} \quad D_{\text{max}} = \frac{5}{12}$

d) 2. B. S EIN

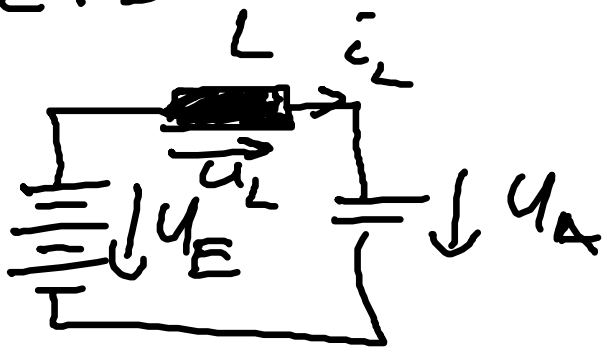

$$U_E = L \frac{d\tilde{i}_L}{dt} + U_A$$

↓ linear

$$U_E = L \frac{D\tilde{i}_L}{Dt} + U_A$$

$$\downarrow DT_S = D \frac{1}{f_s}$$

$$U_E = L \frac{D\tilde{i}_L}{D \frac{1}{f_s}} + U_A \quad \Delta\tilde{i}_L = \frac{U_E D (1-D)}{L f_s}$$

$D U_E \rightarrow$

e)



2.)

a) l klein \rightarrow η klein

$$l(\eta) = I_0 \left[1 + \frac{\alpha n r F}{R T} \eta - 1 + \frac{(1-\alpha) n r F}{R T} \eta \right]$$

$$I(\eta) = I_0 \frac{nF}{RT} \mathcal{L}$$

Einheit?


$$\left[I_0 \frac{nF}{RT} \right] = 1 \text{ S} = 1 \frac{1}{\Omega}$$

$$\Rightarrow R_{DS} = \frac{RT}{I_0 nF} \quad \text{Doppelschichtwiderstand}$$

Korrektur der BVG:

$$I(\eta) = I_0 \left(e^{\frac{\alpha nF}{RT} \mathcal{L}} - e^{-\frac{(1-\alpha)nF}{RT} \mathcal{L}} \right)$$

b)

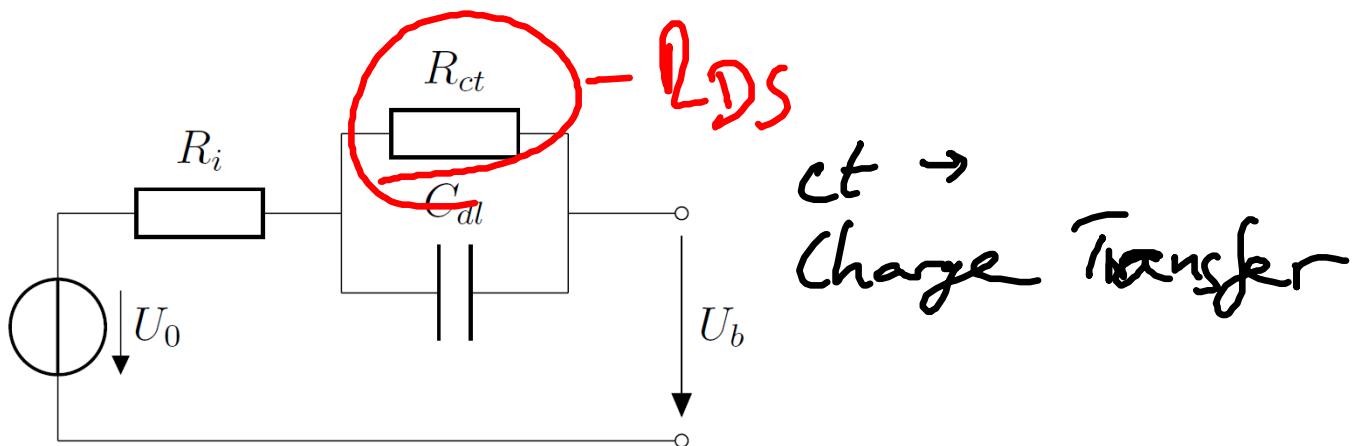

$$c) \quad n_{\text{serie}} = \frac{U_{\text{bat}}}{U_N} = 33 \text{ Zellen}$$

Mindestanzahl:

$$n_{\text{ges}} = \frac{s \cdot E'}{C_N \cdot u_N} = 1730 \text{ Zellen}$$



$$n_{\text{Parallel}} = \frac{n_{\text{ges}}}{n_s} = 53 \text{ Stacks parallel}$$

d)

$$I_{\text{Strang}} = \frac{I_{\text{bat}}}{n_p} = \frac{P_N / u_{\text{bat}}}{n_p}$$
$$= \frac{P_N}{u_N \cdot n_s \cdot n_p} = 3,7 \text{ A}$$

⚡
> 2,5 A
(1C-Rate)

e)

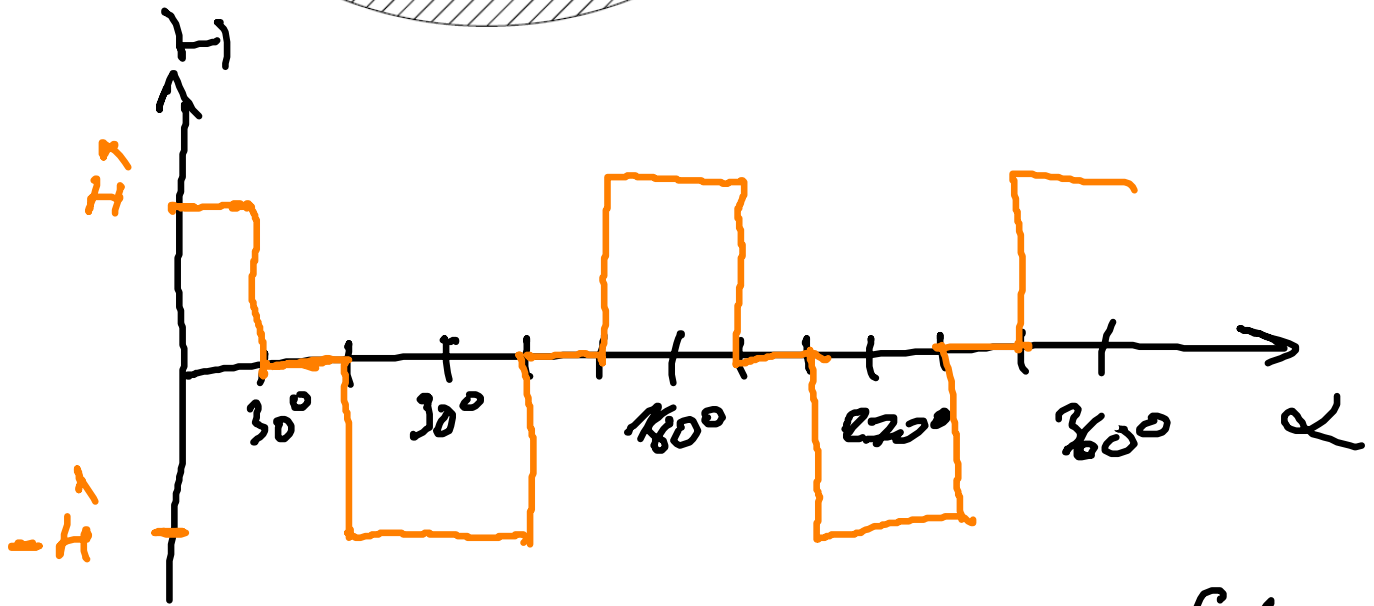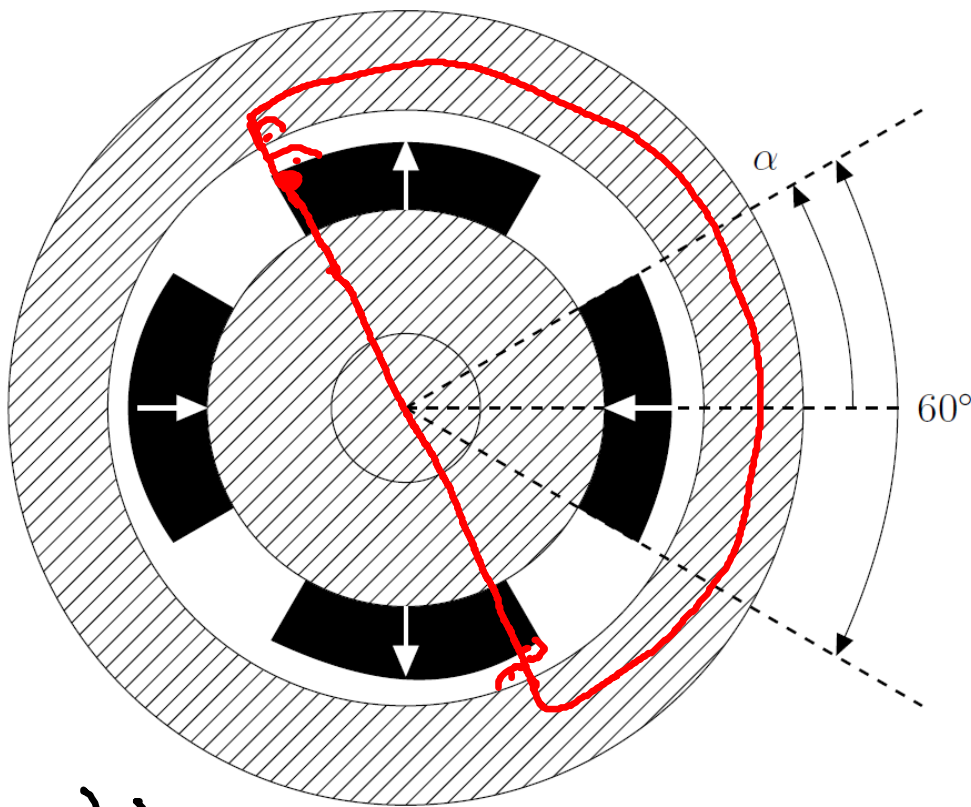

b) Scherungsgerade $B_{PM} = f(H_{PM})$

$$\ominus = wI = \int \vec{H} d\vec{s}$$

$$wI = H_{PM} l_{PM} + \cancel{H_{FE_R} l_{FE_R}} + H_{PM} l_{PM} + H_{\delta} \delta + \cancel{H_{FE_S} l_S} + H_{\delta} \delta$$

$$wI = 2H_{PM} l_{PM} + 2H_{\delta} \delta$$

$$(i) \mu_0 H_{\delta} = B_{\delta} \quad (ii) \quad \phi_{\delta} = \phi_{PM}$$



$$A_{\delta} B_{\delta} = A_{PM} B_{PM}$$

$$B_{\delta} = \frac{A_{PM}}{A_{\delta}} B_{PM}$$

$$\Rightarrow B_{PM} = \frac{\mu_0 A_{\delta}}{2A_{PM} \delta} (wI - 2H_{PM} l_{PM})$$

$$B_{PM} = -\mu_0 \frac{l_{PM}}{\delta} H_{PM}$$
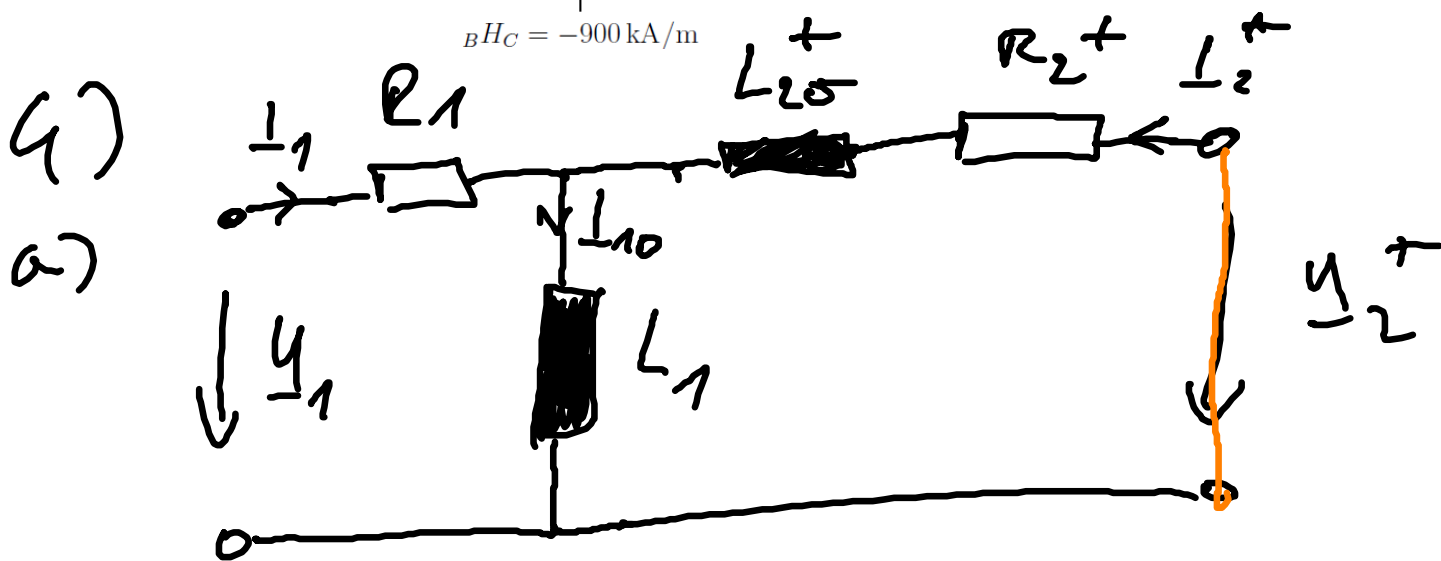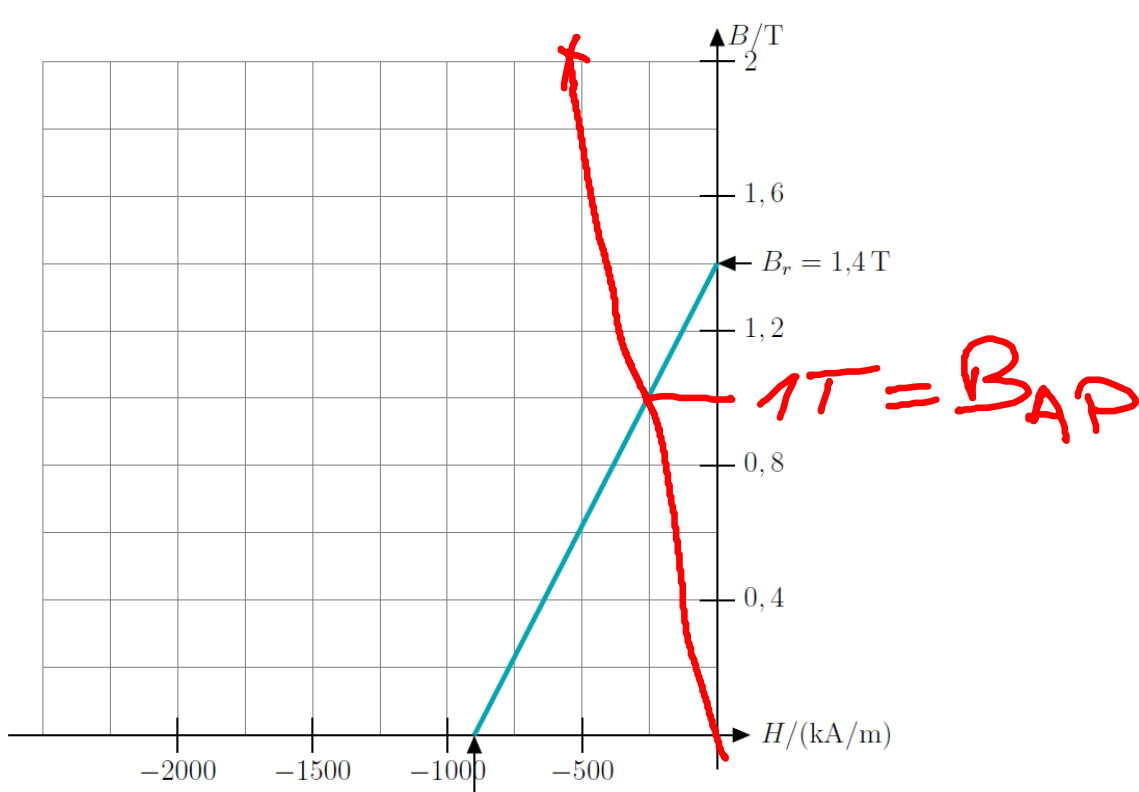
$$B_{PM} = 2T \quad \Rightarrow \quad H_{PM} = -530,52 \frac{kA}{m}$$



b) $I_2^+ = \bar{u}^+ I_2$
 $I_2^+ = \frac{I_2}{\bar{u}^+}$
 $L_{20}^+ = L_1 \frac{\sigma}{1 - \sigma} = (\bar{u}^+)^2 L_2 - \bar{u}^+ L_1$
 $R_2^+ = (\bar{u}^+)^2 R_2$

c) Im Kurzschlussfall:


$$\frac{u_{NK}}{I_{NK}} = \underline{z}_K = R_1 + \frac{j\omega L_1 (R_2 + j\omega L_{2\sigma})}{j\omega L_1 + R_2 + j\omega L_{2\sigma}}$$

$\sigma \ll 1$ für fast alle Trafos

$$L_{2\sigma}^+ = L_1 \frac{\sigma}{1-\sigma} \approx \sigma L_1 \Rightarrow L_{2\sigma}^+ \ll L_1$$

$$\Rightarrow |j\omega L_1| \gg |R_2 + j\omega L_{2\sigma}^+|$$
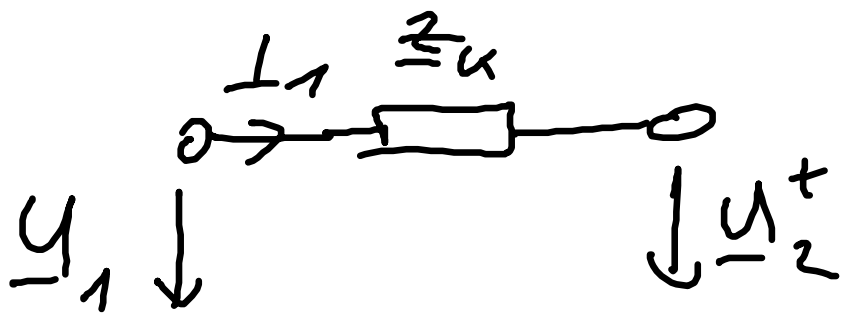
$$\Rightarrow \underline{z}_K = R_1 + R_2 + j\omega L_{2\sigma}^+$$



0-----0

d) $P_{1k} = 3R_1 (I_{1k})^2 + 3R_2^+ (I_{2k}^+)^2$
 $= 3R_1 I_{1k}^2 + 3R_2 (\ddot{u}^+)^2 \left(\frac{I_{2k}}{\ddot{u}^+} \right)^2$

$$R_2 = \frac{P_{1k} - 3R_1 I_{1k}^2}{3 I_{2k}^2} = 0,8 \Omega$$

$$R_2^+ = (\ddot{u}^+)^2 \cdot R_2 = 64,8 \Omega$$

$$\frac{|U_{1k}|}{|I_{1k}|} = |Z_k| = \sqrt{(R_1 + R_2^+)^2 + (\omega L_{20}^+)^2}$$

$$L_{20}^+ = 39,54 \text{ mH}$$

$$\Rightarrow \sigma \approx \frac{L_{20}^+}{L_1} = 0,034$$