

Lösung zu Aufgabe 1:

$$a) \quad \underline{Z}_V = \frac{U_{NV}^2}{S_{NV}} \cdot e^{-j \arccos \varphi_V} = \frac{(690 \text{ V})^2}{110 \text{ kVA}} \cdot e^{-j \arccos 0,85} = 4,328 \Omega \cdot e^{-j 31,8^\circ}$$

$$R_{V,Y} = Z_V \cdot \cos \varphi_V = 4,328 \Omega \cdot 0,85 = 3,679 \Omega$$

$$X_{V,Y} = Z_V \cdot \sin \varphi_V = Z_V \cdot \sqrt{1 - \cos^2 \varphi_V} = 4,328 \Omega \cdot \sqrt{1 - 0,85^2} = 2,280 \Omega$$

$$b) \quad \ddot{u} = \frac{U_{NT1}}{U_{NT2}} = \frac{220 \text{ kV}}{690 \text{ V}} = 319$$

$$X_{2\sigma}' = \ddot{u}^2 \cdot X_{2\sigma} = 319^2 \cdot 0,25 \Omega = 25,4 \text{ k}\Omega$$

$$\underline{Z}_T' = jX_{1\sigma} + jX_{2\sigma}' = j30 \text{ k}\Omega + j25,4 \text{ k}\Omega = j55,4 \text{ k}\Omega$$

$$c) \quad \underline{Z}_{V,Y}^* = R_{V,Y}^* - jX_{V,Y}^* = \ddot{u}^{*2} \cdot (R_{V,Y}^* - jX_{V,Y}^*) = 300^2 \cdot (3 \Omega - j1,8 \Omega) = (270 - j162) \text{ k}\Omega$$

$$\underline{I}_{L,1} = \frac{U_{G,\text{Strang}}}{\underline{Z}_G + \underline{Z}_T^* + \underline{Z}_{V,Y}^*} = \frac{\frac{220 \text{ kV}}{\sqrt{3}}}{(12 + j20) \text{ k}\Omega + j50 \text{ k}\Omega + \text{k}\Omega(270 - j162)} = 0,429 \text{ A} \cdot e^{j18,07^\circ}$$

$$I_{L,2} = \ddot{u} \cdot I_{L,1} = 300 \cdot 0,429 \text{ A} = 129 \text{ A}$$


$$d) \quad \varphi_{L,2} = \varphi_{L,1} + 5 \cdot 30^\circ = 168,07^\circ$$

$$U_{V,\text{Strang}} = I_{L,2} \cdot \sqrt{R_{V,Y}^2 + X_{V,Y}^2} = 451,31 \text{ V}$$

Die kapazitive Komponente wirkt spannungserhöhend.

Lösung zu Aufgabe 2:

a) $p = 1$

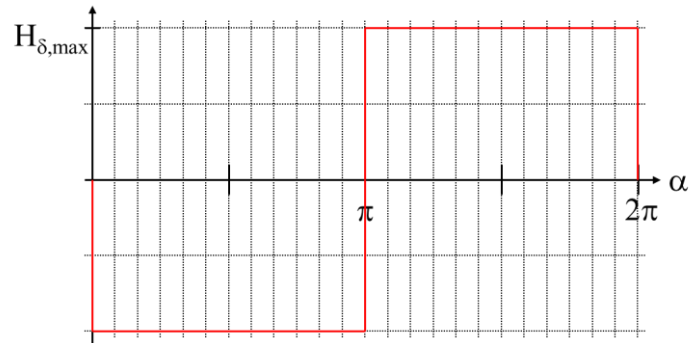


b) $\Theta = w_1 \cdot I_1 = 2 \cdot H_{\delta, \max} \cdot l_\delta$

$$H_{\delta, \max} = \frac{w_1 \cdot I_1}{2 \cdot l_\delta} = \frac{213 \cdot 12 \text{ A}}{2 \cdot 2,5 \text{ mm}} = 511,2 \frac{\text{kA}}{\text{m}}$$

$$B_{\delta, \max} = \mu_0 \cdot H_{\delta, \max} = 4\pi \cdot 10^{-7} \frac{\text{Vs}}{\text{Am}} \cdot 5,112 \cdot 10^5 \frac{\text{A}}{\text{m}} = 0,642 \text{ T}$$

c)

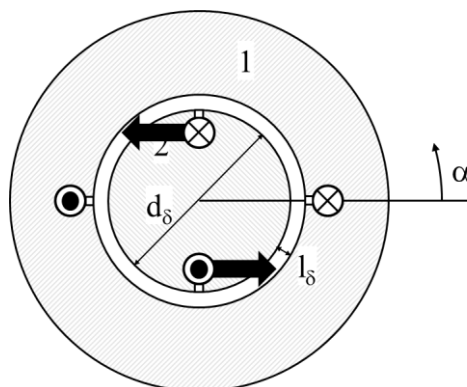

$$F = w_2 \cdot I_2 \cdot l_{\text{Fe}} \cdot B_{\delta, \max} = 5 \cdot 40 \text{ A} \cdot 0,3 \text{ m} \cdot 0,642 \text{ T} = 38,5 \text{ N}$$

$$M = 2 \cdot F \cdot \frac{d_\delta}{2} = F \cdot d_\delta = 38,5 \text{ N} \cdot 0,12 \text{ m} = 4,622 \text{ Nm}$$

d) $U_i \sim n$ (Drehzahl)

$$I_a \sim M$$
 (Drehmoment)

in der Spannungsquelle (Produkt aus Spannung und Strom durch die Quelle, motorisch positiv gezählt)

Lösung zu Aufgabe 3:


$$n_0 = \frac{f_1}{p} = \frac{400 \text{ Hz}}{3} = 133 \text{ s}^{-1} = 8000 \text{ min}^{-1}$$

$$n_N = n_0 \cdot (1 - s_N) = 8000 \text{ min}^{-1} \cdot (1 - 0,05) = 7600 \text{ min}^{-1}$$

$$M_K = \frac{3 \cdot p \cdot U_{\text{Strang}} \cdot I_{K,\text{Strang}} \cdot \cos \varphi_K}{2 \cdot \pi \cdot f_1} = \frac{3 \cdot 3 \cdot 115 \text{ V} \cdot 375 \text{ A} \cdot \cos(-80^\circ)}{2 \cdot \pi \cdot 400 \text{ Hz}} = 26,82 \text{ Nm}$$

$$\frac{M_N}{M_{\text{Kipp}}} = \frac{4,1 \text{ cm}}{8,6 \text{ cm}} = 0,48$$

Skizze s. nächstes Blatt

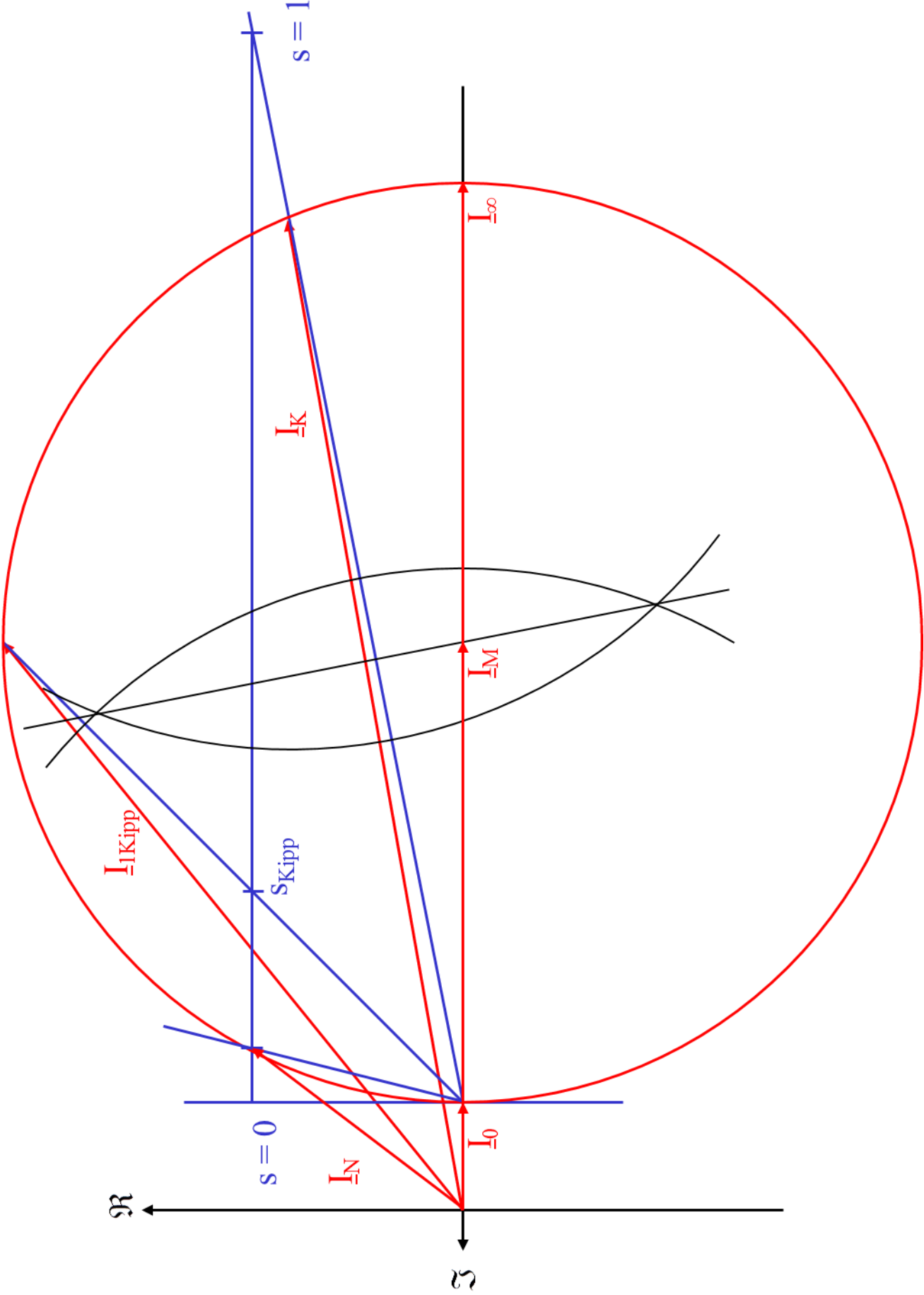

Lösung zu Aufgabe 4:

$$a) \quad S_{el,max} = U_N \cdot I_{max} = 230 \text{ V} \cdot 6,35 \text{ A} \cdot 0,87 = 1462 \text{ VA}$$

$$\eta_{max} = \frac{P_{max}}{P_{el,max}} = \frac{P_{max}}{S_{el,max} \cdot \cos \varphi_{max}} = \frac{1100 \text{ W}}{1462 \cdot 0,87} = 86,6 \%$$


$$M_{max} = \frac{P_{max}}{2\pi \cdot n_{max}} = 5,8 \text{ Nm}$$

$$b) \quad Q_{el,max} = S_{el,max} \cdot \sin \varphi_{max} = S_{el,max} \cdot \sqrt{1 - \cos^2 \varphi_{max}} = 721 \text{ var}$$

$$(L_a + L_f) = \frac{Q_{el,max}}{\omega_N \cdot I_{max}^2} = 56,8 \text{ mH}$$

$$(R_a + R_f) = \frac{P_{el,max} - P_{max}}{I_{max}^2} = 4,21 \Omega$$

c)

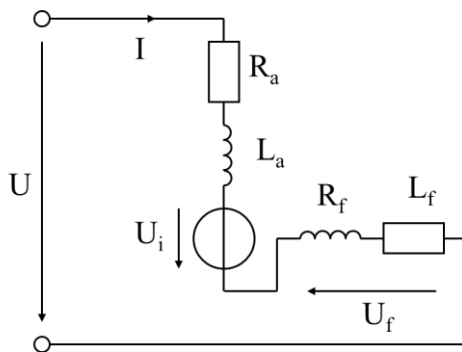

$$U_{i,max} = \frac{P_{max}}{I_{max}} = 173,22 \text{ V}$$

$$k \cdot k' = \frac{k \cdot \Phi_{max}}{I_{max}} = \frac{U_{i,max}}{I_{max} \cdot n_{max}} = 0,9 \Omega$$

d)

$$M_N = \frac{k\Phi}{2\pi} \cdot I_N = \frac{k \cdot k'}{2\pi} \cdot I_N^2 \Rightarrow$$

$$I_N = \sqrt{\frac{2\pi M_N}{k \cdot k'}} = 2,64 \text{ A}$$

$$U_N = \sqrt{(k \cdot k' \cdot I_N \cdot n_N + (R_a + R_f) \cdot I_N)^2 + (\omega \cdot (L_a + L_f) \cdot I_N)^2} = 49,46 \text{ V} (41,75 \text{ V})$$

Normalwaschgang